


## Assignment 4.1

### Verilog Design of 8 x 16 Register File

#### Register File Specification:

- A register file consists of 8 registers, each register of 16-bit width.
- The register file has read data bus(**RdData**), write data bus(**WrData**) and one address bus (**Address**) used for both read and write operations.
- Each register can be read and written by applying a register address to be accessed.
- Only one operation (read or write) can be evaluated at a time.
- Write Operation is done only when **WrEn** is high
- Read operation is done only when **RdEn** is high.
- Read and Write operations are done on positive edge of **Clock**
- All the registers are cleared using Asynchronous **active low Reset** signal

#### Block Interface: -

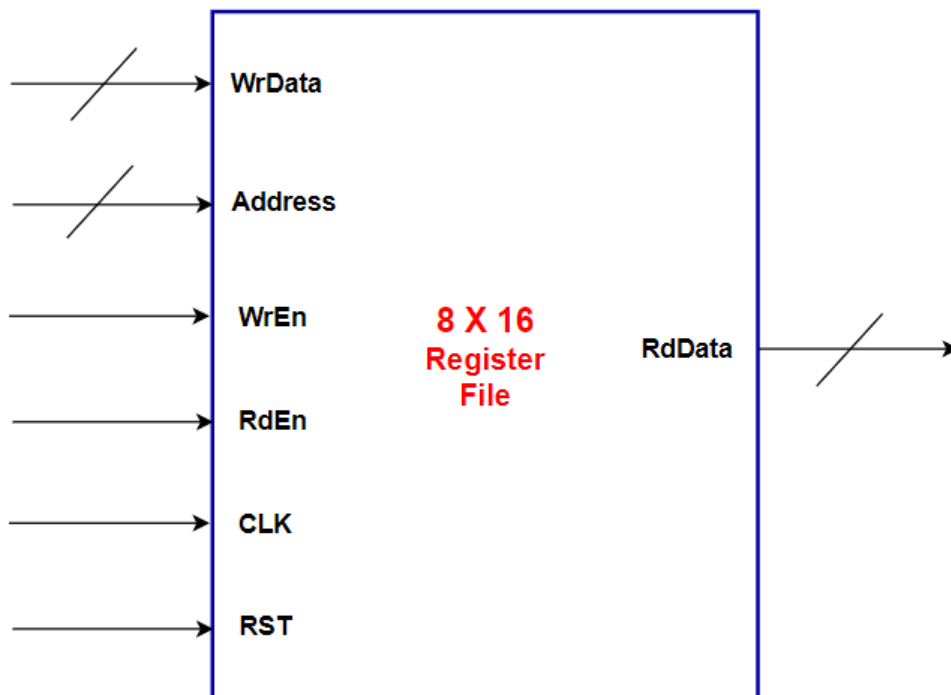

**Hint:** To clear the register using asynchronous reset signal, you need to put the reset condition the first one as following example

```
always @(posedge clock or posedge rst)
begin
    if(rst)
    begin
        Reg_File[0] <= 16'b0 ;
        Reg_File[1] <= 16'b0 ;
        .....
        Reg_File[7] <= 16'b0 ;
    end
else
    .....
```

**Hint:** You do not need to make this code parameterized for simplicity.

**Hint:** Let Session\_4/Lab\_V\_4.2 is your starting point for this assignment

Requirements: -

- 1- Design a register file with the above specifications using Verilog language and determine Read and Write data buses width and address bus width.
- 2- Write a testbench to validate your design including at least 4 scenarios two for writing in the registers and two for reading from the registers.